

MBA Fast Corrector Power Supply Development

November 18, 2015

Byeong. Song*

Gary Sprau

Ju Wang

* No longer with APS



Outline

- Power supply requirement for the APS-U
- Technical requirement and challenges
- Choice of power circuit and regulation algorithm
- Prototype design
- Initial test results

Scope of APS-U Storage Ring Power Supplies

- 2082 power supplies for the APS-U magnets
 - Two large power supplies up to 1000A for L-bend (M1/M2) dipole magnets
 - One thousand 10 ppm stability-class and 230A unipolar DC power supplies for Q-bend (M3/M4) dipole, quadrupole, and sextupole magnets
 - 760 ± 15 A DC bipolar power supplies for trim/correction and skew quad coils
 - **320 ± 15 A bipolar power supplies for fast correctors**
- 400 power supply controllers
 - 200 Unipolar power supply controllers
 - 200 Bipolar power supply controllers
- Pre-installation test
 - All the power supplies and the power supply controllers will be 100% tested in a temperature-elevated environment before the installation starts

New SR requires 2082 power supplies and 400 power supply controllers. All need to be pre-tested and ready before shutdown starts.

Fast Corrector PS Specifications and Parameters

Specifications/Design Paramters	Fast Corr PS	Exiting PS*	Unit
Maximun operating current	±13	±150	A
Maximun output voltage	40	40	V
Maximun output power	0.52	6	kW
Current stability (AC RMS)	TBD	300	ppm
Initial accuracy after installation	100		ppm
Magnet-to-magnet repeatability	100	700	ppm
Reproducibility after shutdown	10	600	ppm
Small-signal -3dB bandwidth	10		kHz
Current ripple	TBD	1000	ppm
Voltage ripple	TBD		ppm
Magnet inductance	16.5	3.48/4.28	mH

* Parameters from 1992 power supply design review

- Fast Communications Requirements
 - 22.6 kHz update rate
 - 10 μs latency


Challenges and Issues

- Fast corrector magnet is very inductive
 - 16.5 mH in the design by BNL
 - High impedance at 10 kHz

$$Z = \omega L = 2\pi fL = 2\pi \times 10000 \times 0.0165 = 1036.7 \Omega$$


- For 130 mA (1% of full rating) peak-to-peak current at 10 kHz, required peak-to-peak voltage is
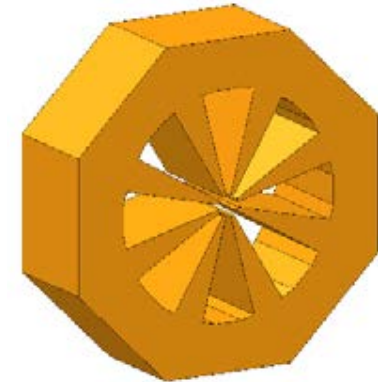
$$V = Z \times I = 1036.7 \times 0.13 = 134.7 V$$



8 pole fast corrector magnet

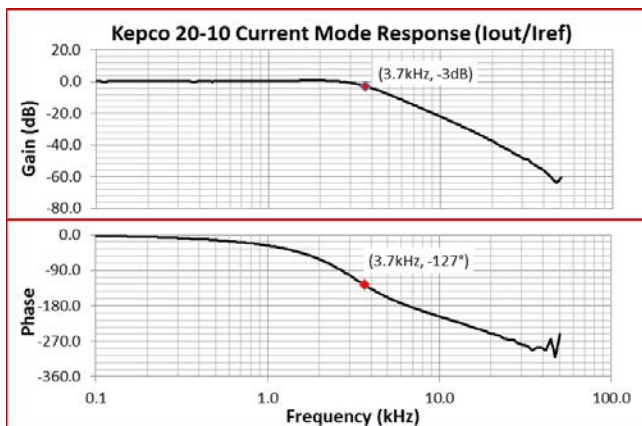- No commercial bipolar power supplies meet this requirement



Example:

Kepco 20-10 ($\pm 20V$, $\pm 10A$) linear power supply
With a 10 mH load, -3dB at 3.7 kHz

R&D Goals


- Choose appropriate power supply circuit topology
- Choose appropriate hardware for the power circuit
- Design control loop
- Stay within constraints
 - Use existing 40V DC bus
- Deliver a 75 mA peak-to-peak current at 10 kHz
- Keep the design simple for reliability

Some of Basic Power Circuits

■ Switching mode power supplies


– Buck converters

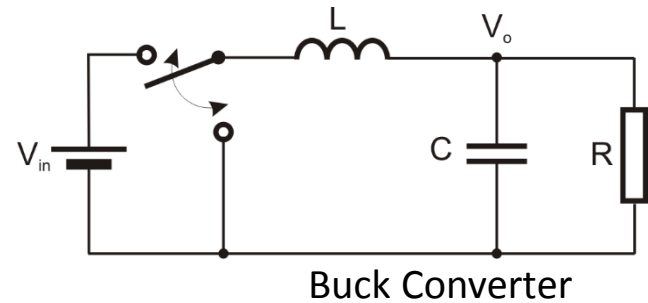- Simple topology
- Output voltage less than input voltage
- Output can be unipolar or bipolar
- All APS storage ring power converters are buck converters



– Boost converter

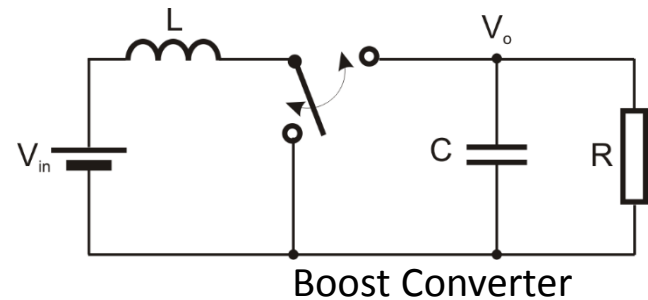- Simple topology
 - Output voltage greater than the input voltage
 - Unipolar output only
- ### – Buck-boost or Boost-buck converters,
- Output voltage can be either higher or lower than the input
 - Output can be unipolar or bipolar




■ Linear power amplifiers

- Works like operational amplifiers
- High bandwidth, hundreds kHz
- High power consumption, good for AC, not good for DC



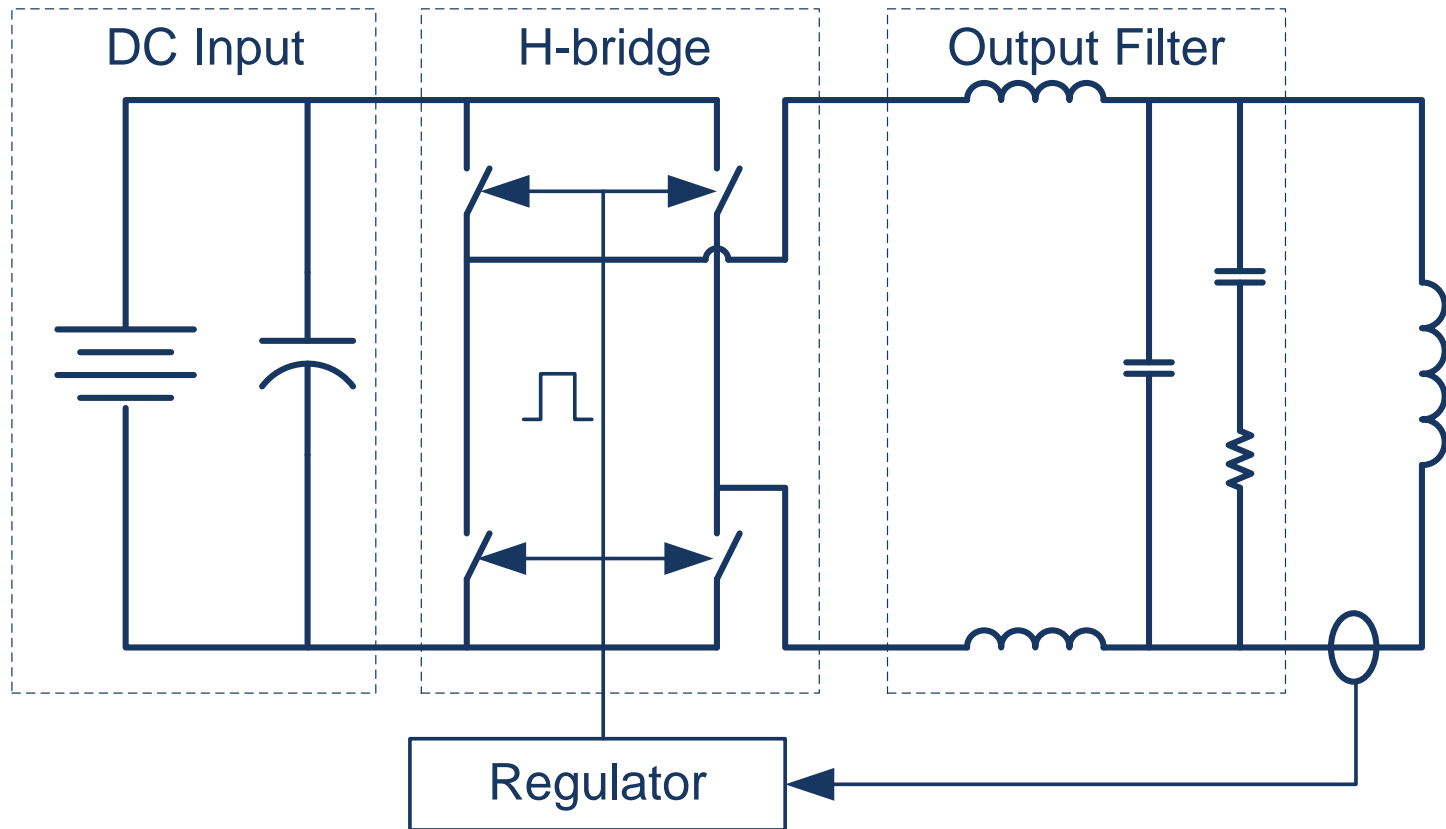Proposed Circuit for Bipolar Power Supply



- An H-bridge with four semiconductor switches
- Bipolar output
- Output voltage \leq input voltage – a buck converter
- Output filter to reduce ripple voltage and ripple current

Semiconductor Switches

■ Discrete MOSFET switches

- Small size
- Low conduction resistance
- Low cost



Example:
IRFB 4610, 100V, 73A,
11 m Ω on resistance
TO-220 package
Less than \$2.50 per MOSFET

■ Switching (class D) amplifiers

- Full bridge package
- Built-in PWM generator
- Built-in gate drive circuit
- Built-in protection circuit
- High conduction losses
- High cost





Example:
APEX SA12, 200V, 15A,
400 m Ω on resistance
200 kHz built-in PWM
\$400 - \$600 per unit



In comparison, existing SR corrector power supplies uses two IGBTs, each rated 600V, 300A, and cost ~ \$200


Power Supply Regulator Design

- Pulse width modulation (PWM) methods
 - A reference signal is compared with a periodic signal
 - Switches under control is turned on or off according to the comparison result
 - There are many PWM methods available
 - The simplest uses sawtooth or triangular waveforms
 - The power supply output voltage is proportional to the switch on time during the cycle, a.k.a. duty cycle or duty ratio
- Closed feedback loop for the current regulation
 - Proportional and integral (P-I) compensator
 - Lead-lag compensator to improve high frequency performance

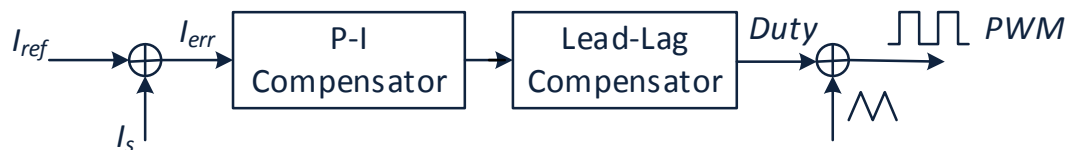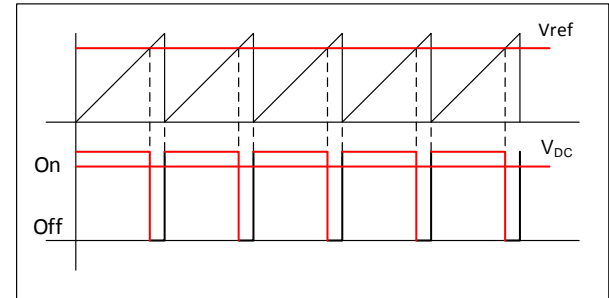


$$\frac{Y}{X} = \frac{(s + z_1)(s + z_2)}{(s + p_1)(s + p_2)}$$

$$|p_1| > |z_1| > |z_2| > |p_2|$$

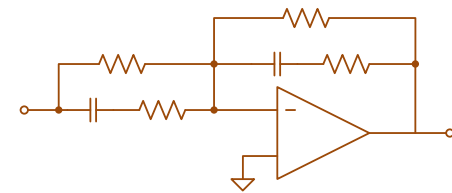

Lead-lag compensator


Sawtooth PWM

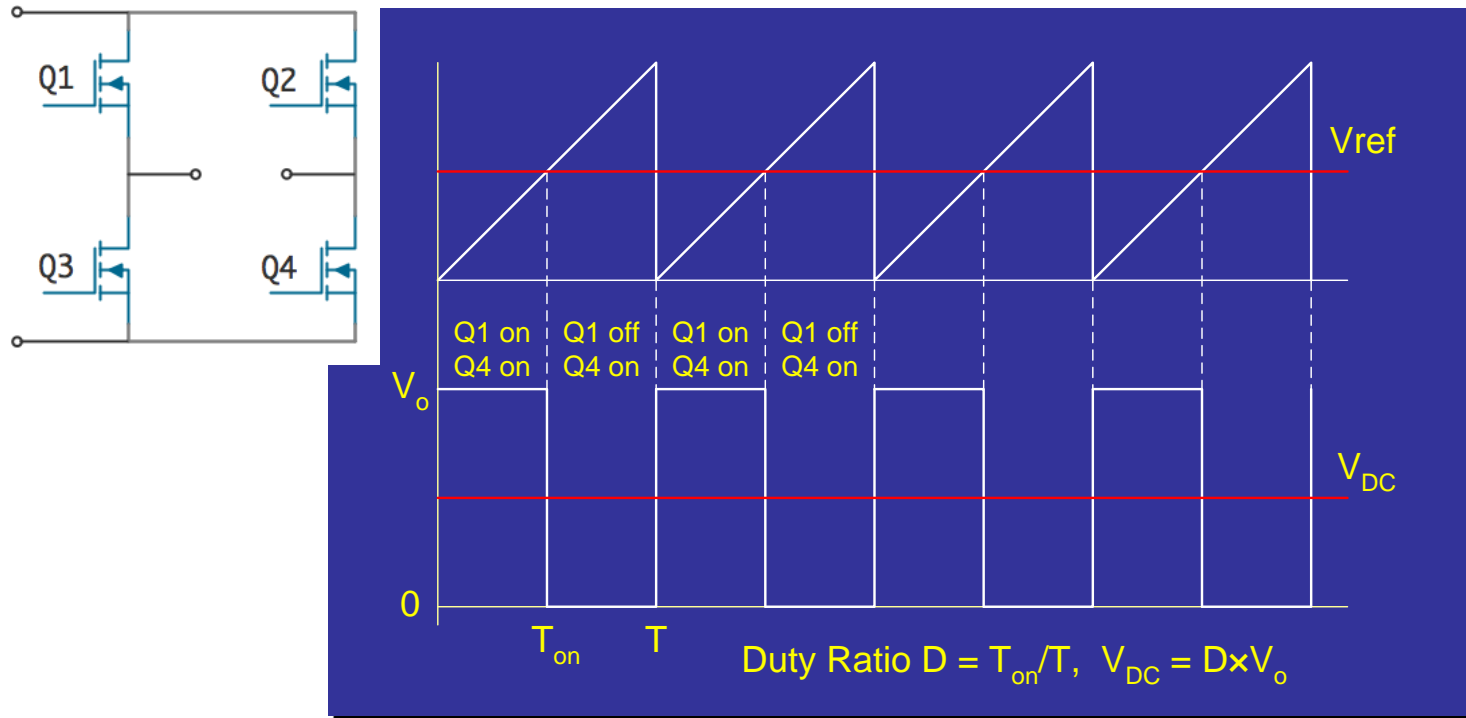

Switch Q1 or Q2 is modulated to regulate the output while switch Q3 or Q4 is held on to control the polarity


- Only two switches are used for a given output polarity
- Very simple and easy to implement
- Does not work well for very small duty ratio or around zero for bipolar output
- Used in the storage ring quad, sext, and original corrector power converters

Unipolar PWM - choice for the design

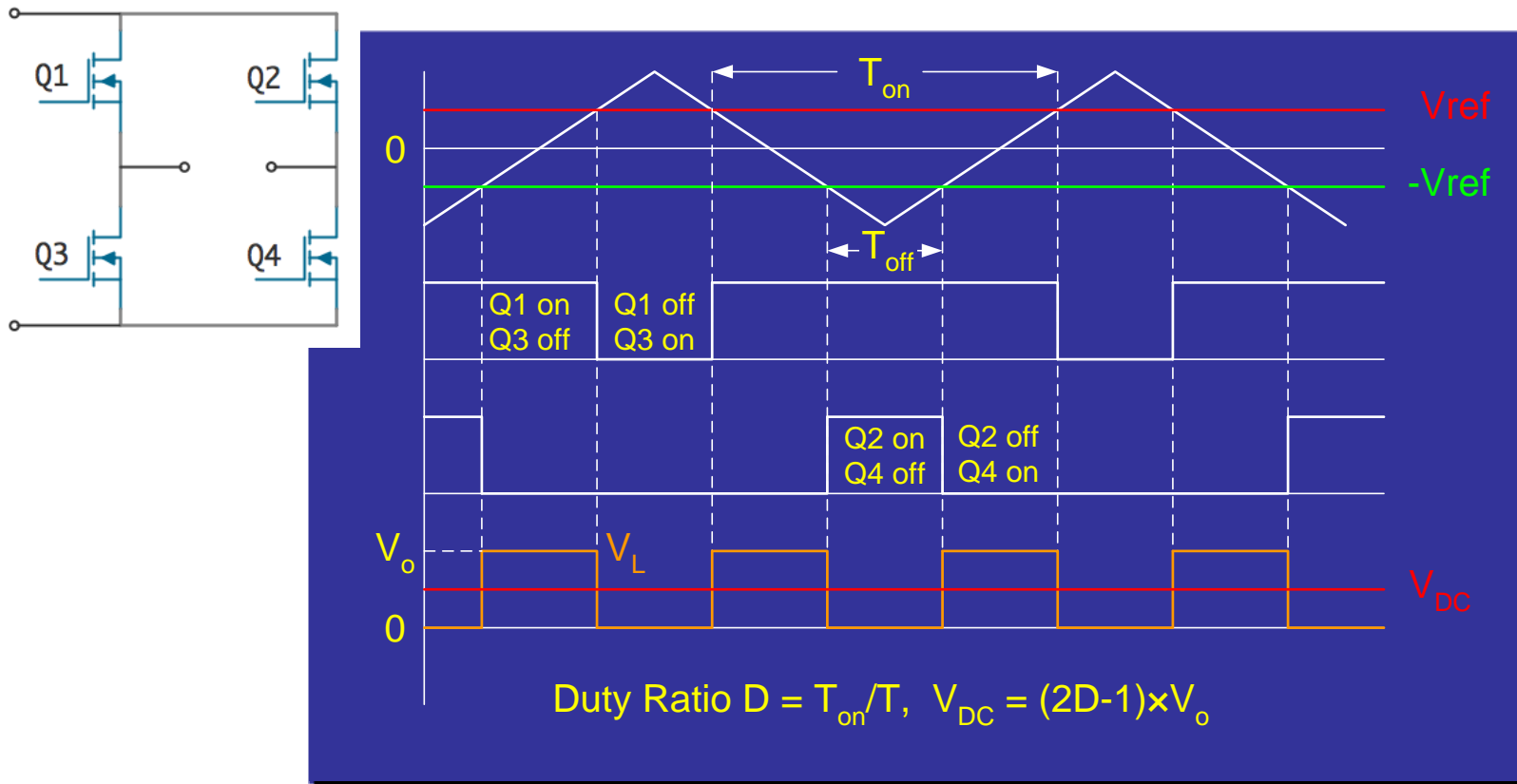


- V_{DC} can be positive or negative
- Ripple frequency is twice the PWM frequency
- Zero output at $D = 0.5$
- Smooth transition around zero

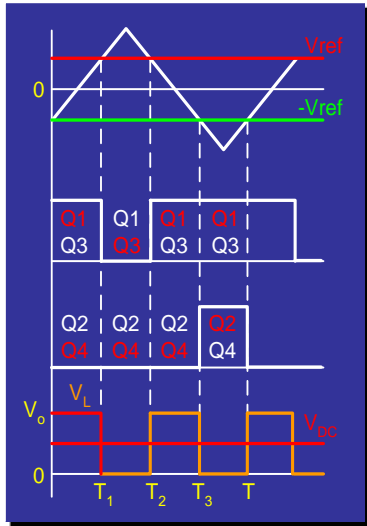
Switching sequence: assume Q1 and Q4 on initially




Positive I , $0 < t < T_1$

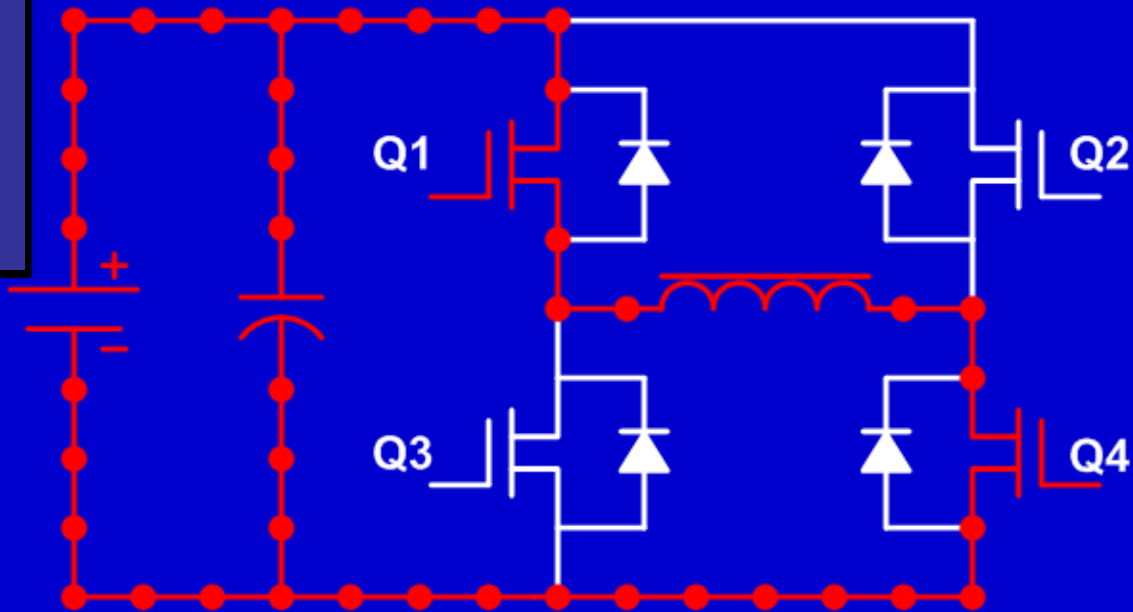

Switching 1: Q1 off and Q3 on

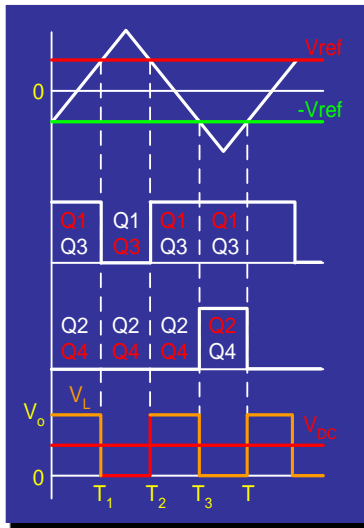


Positive I , $T_1 < t < T_2$

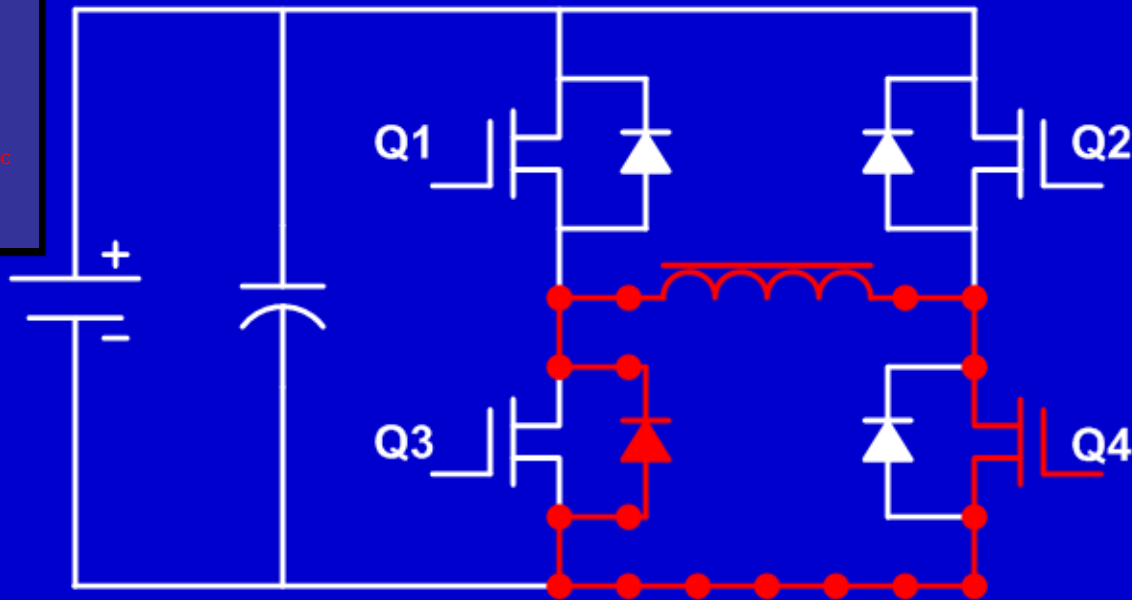


Q3 does not need to be gated on. But, with MOSFETs, gate-on may result in lower conduction losses.



Switching 2: Q1 on and Q3 off

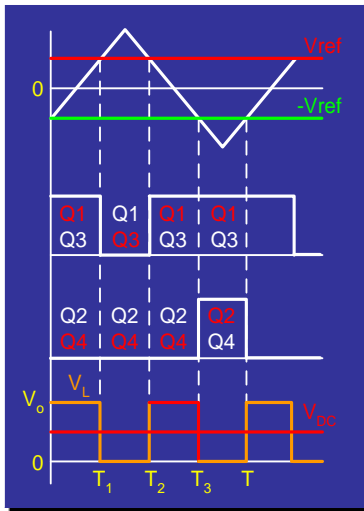


Positive I , $T_2 < t < T_3$

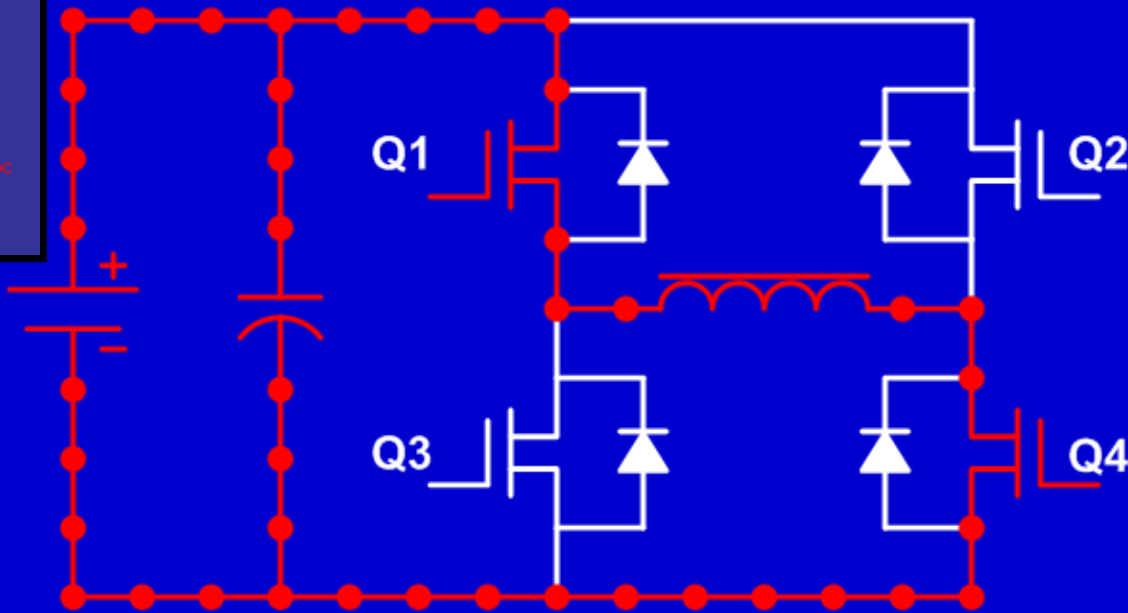


Switching 3: Q4 off and Q2 on

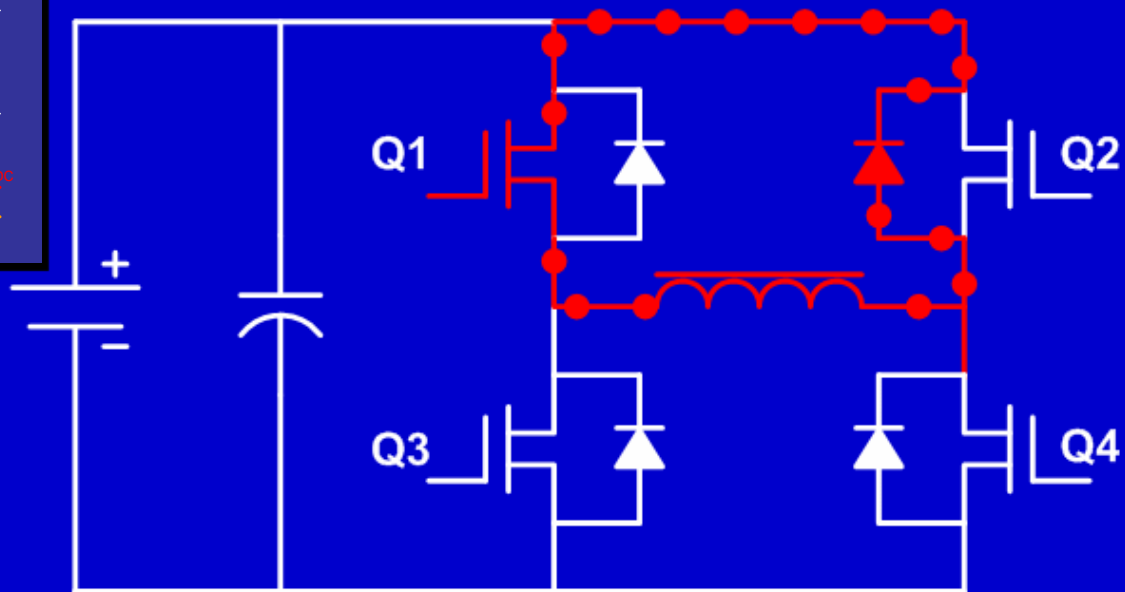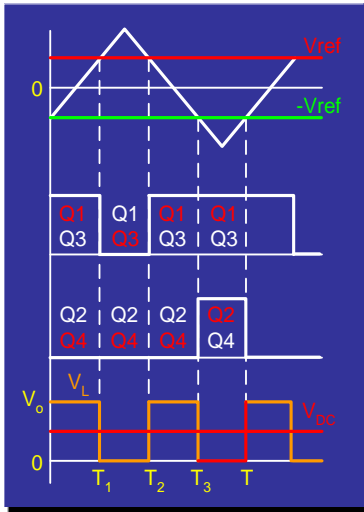


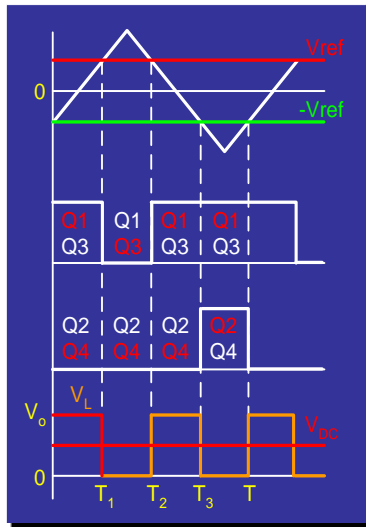
Switching 4: Q4 on and Q2 off, back to initial condition




Positive I , $0 < t < T_1$

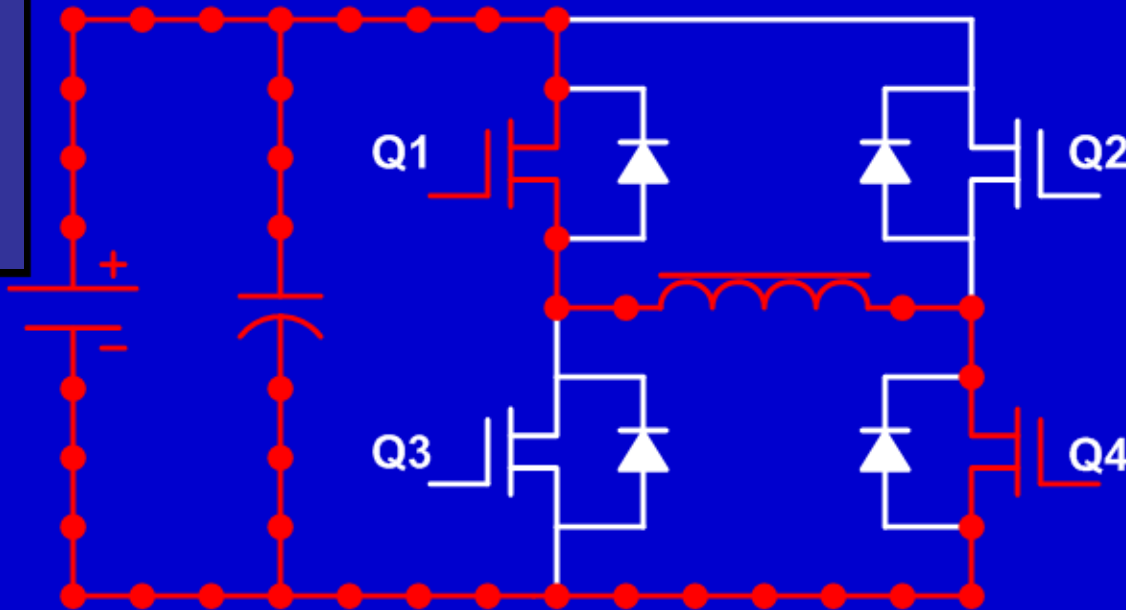

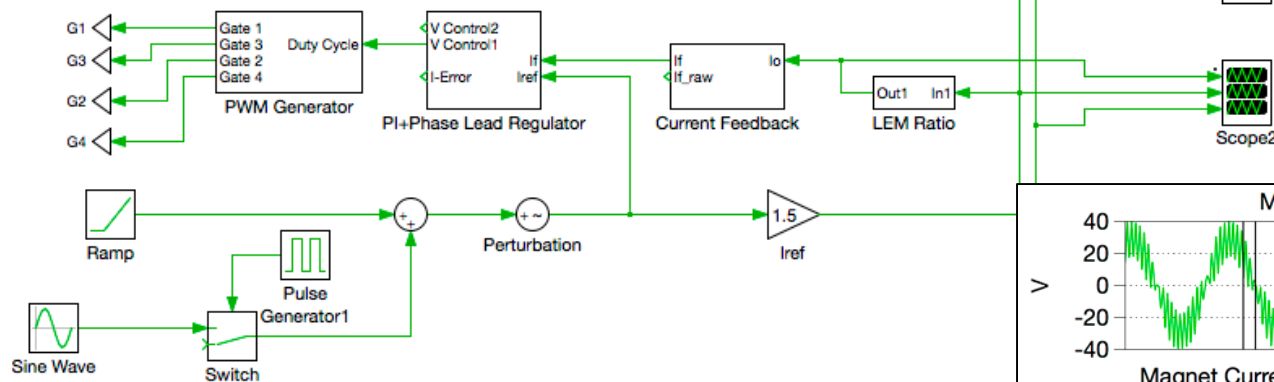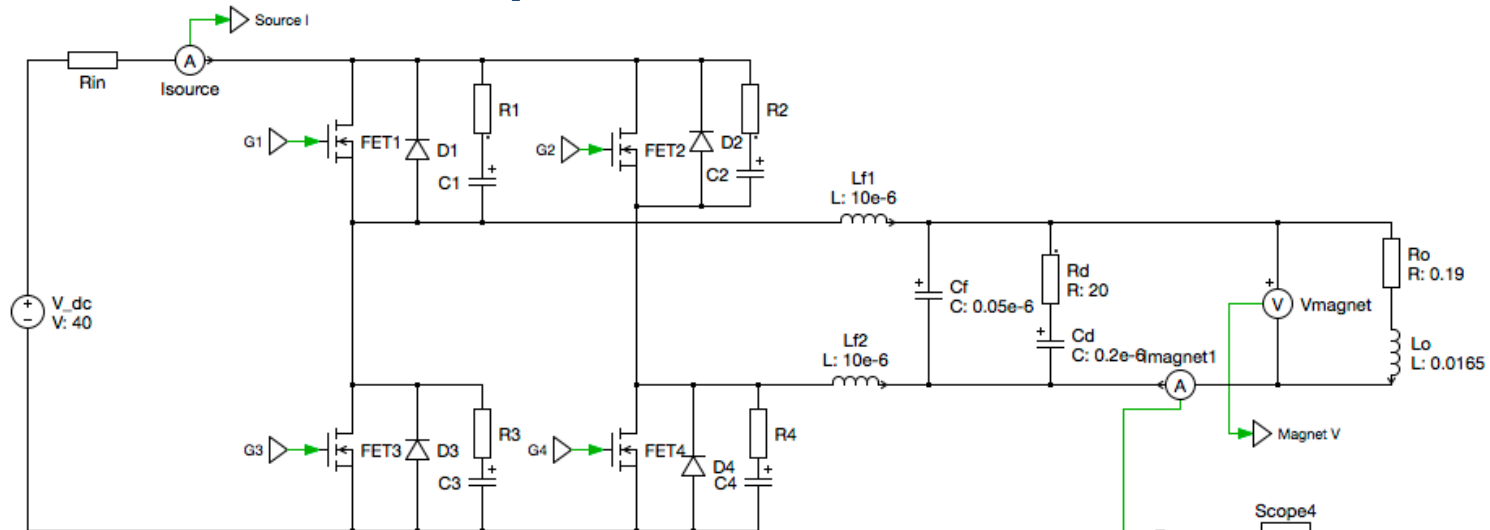
Simulation with PLECS (piecewise linear electrical circuit simulation)



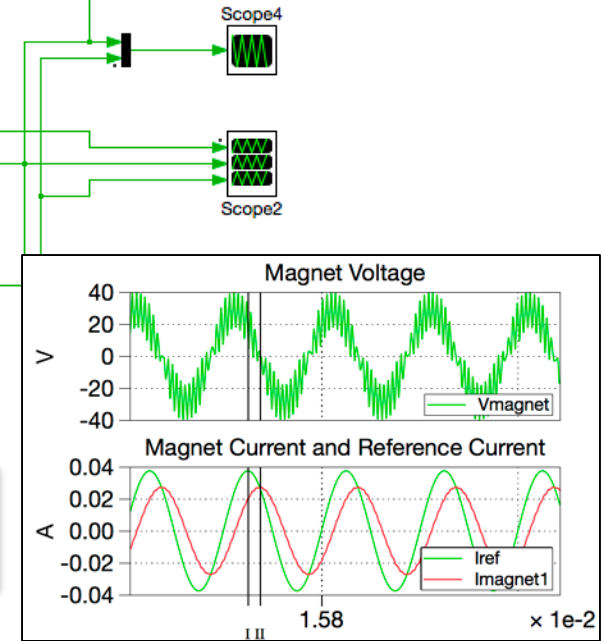
At 10 kHz, 75 mA pk-pk sine reference, output current attenuation -2.05dB, phase shift 44.3°



First Prototype


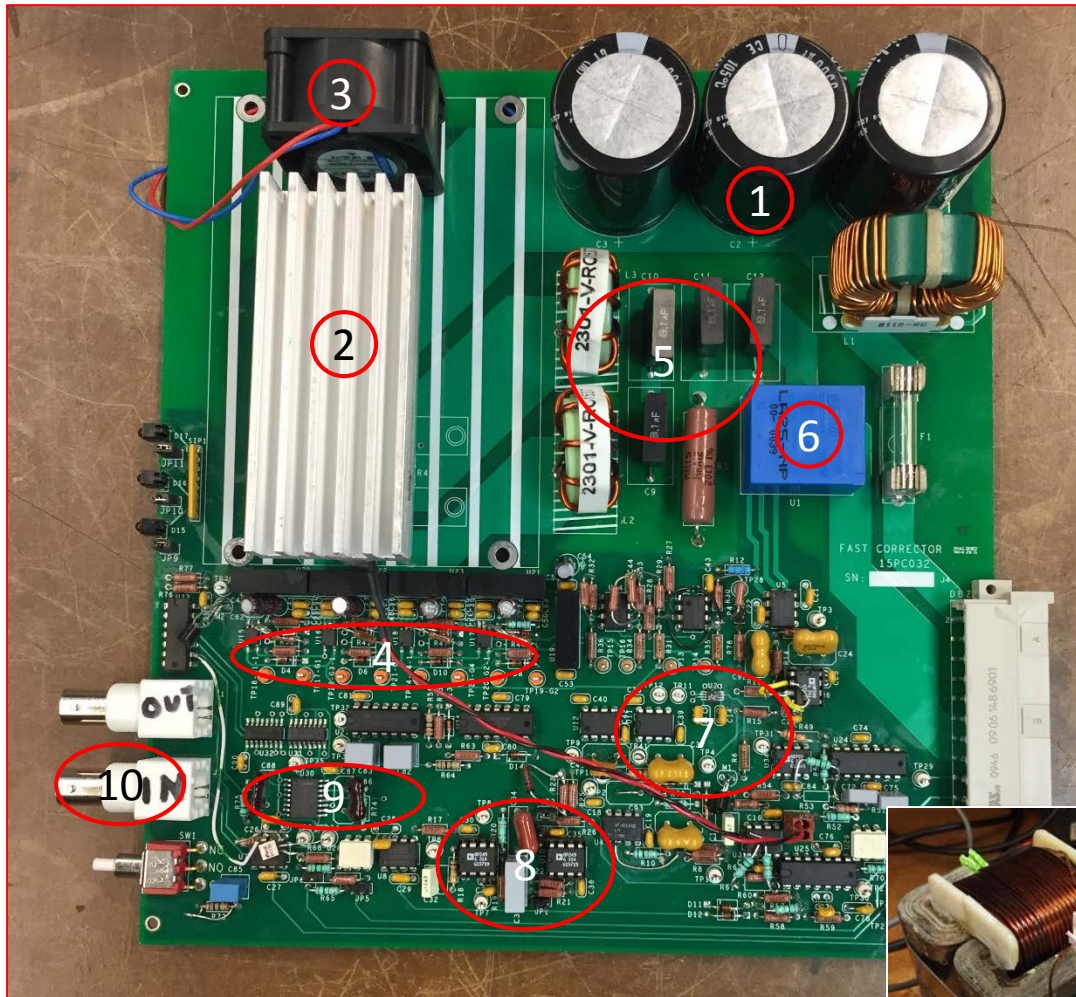


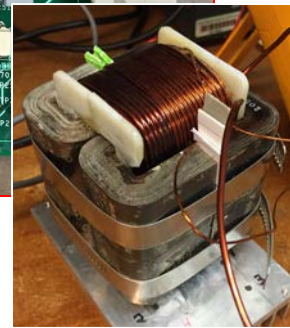1. Input capacitor bank
2. MOSFET heat sink
3. Cooling fan
4. MOSFET gate drive circuit
5. Output filter
6. Current sensor, LEM
7. Triangular waveform generator
8. P-I and lead-lag compensators
9. Interlocks for over current and over temperature
10. Reference input





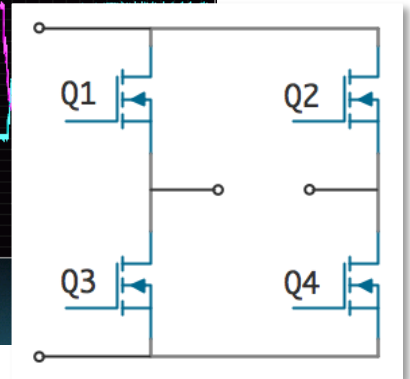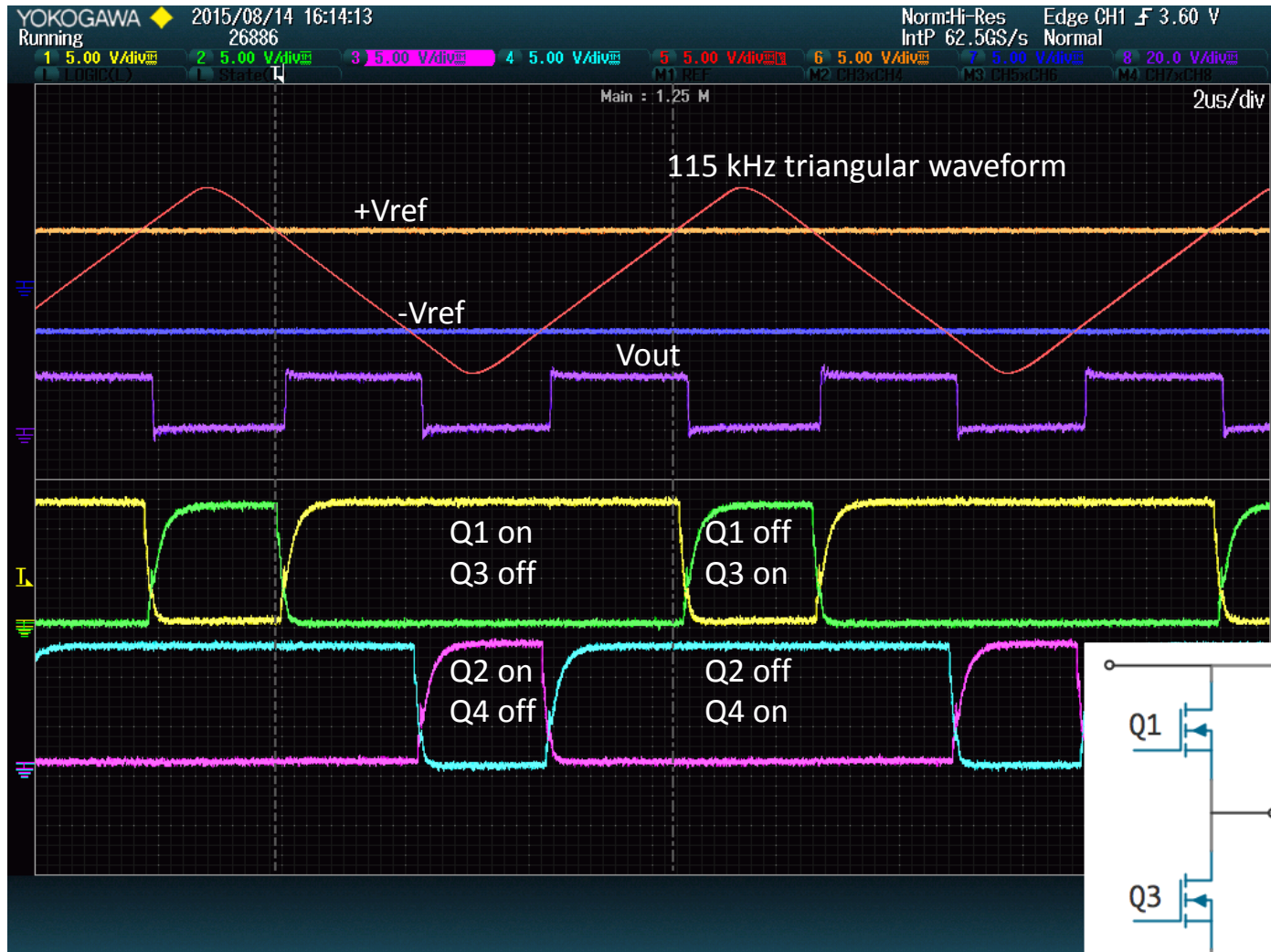16.5 mH high frequency magnet


Initial Test Results - MOSFET Gate Signals



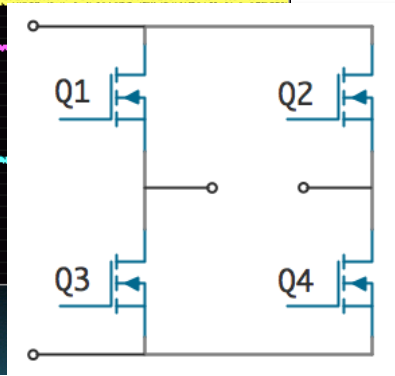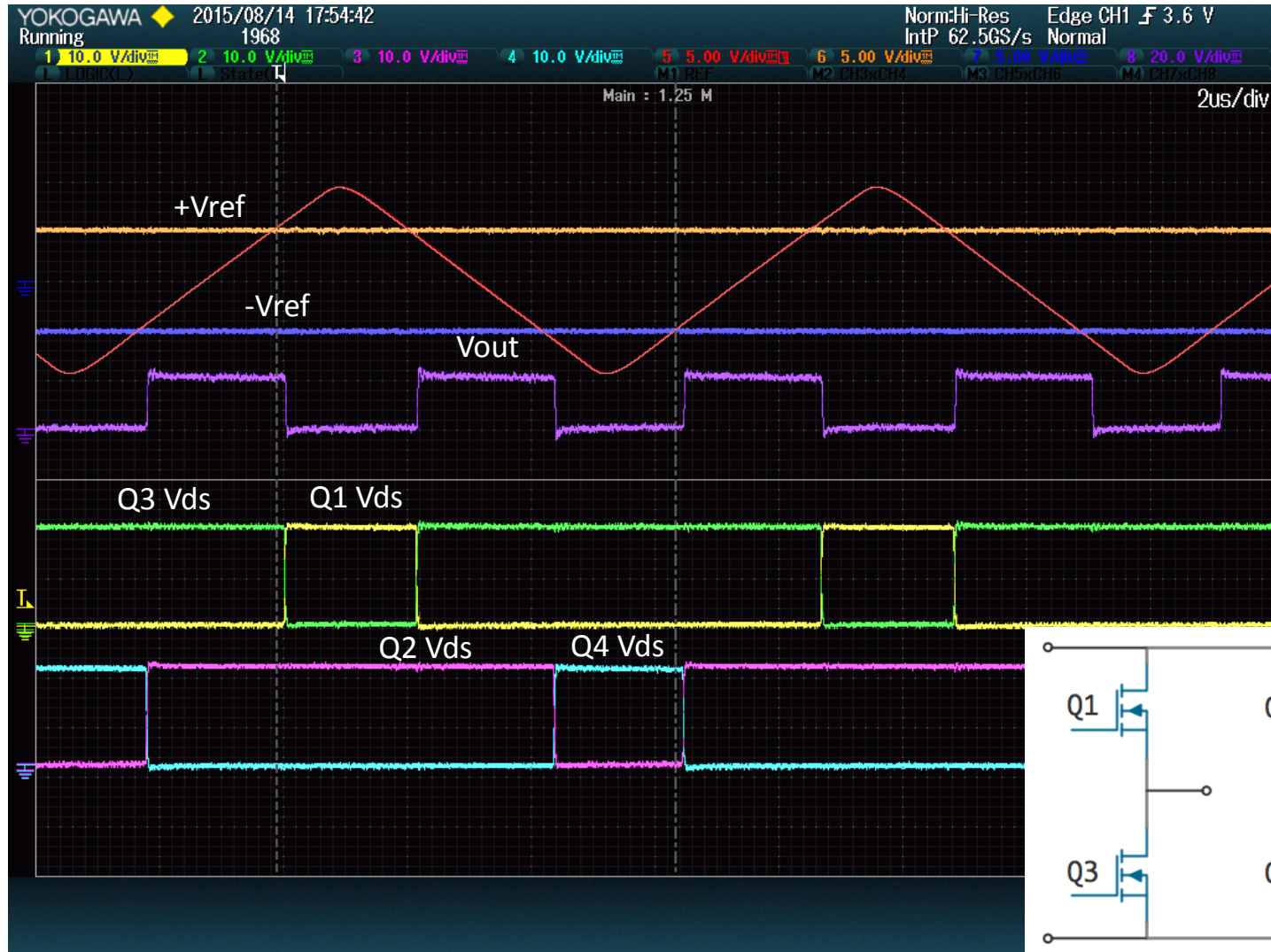MOSFET Drain-Source Voltage - no shoot-through condition




Step Function Response

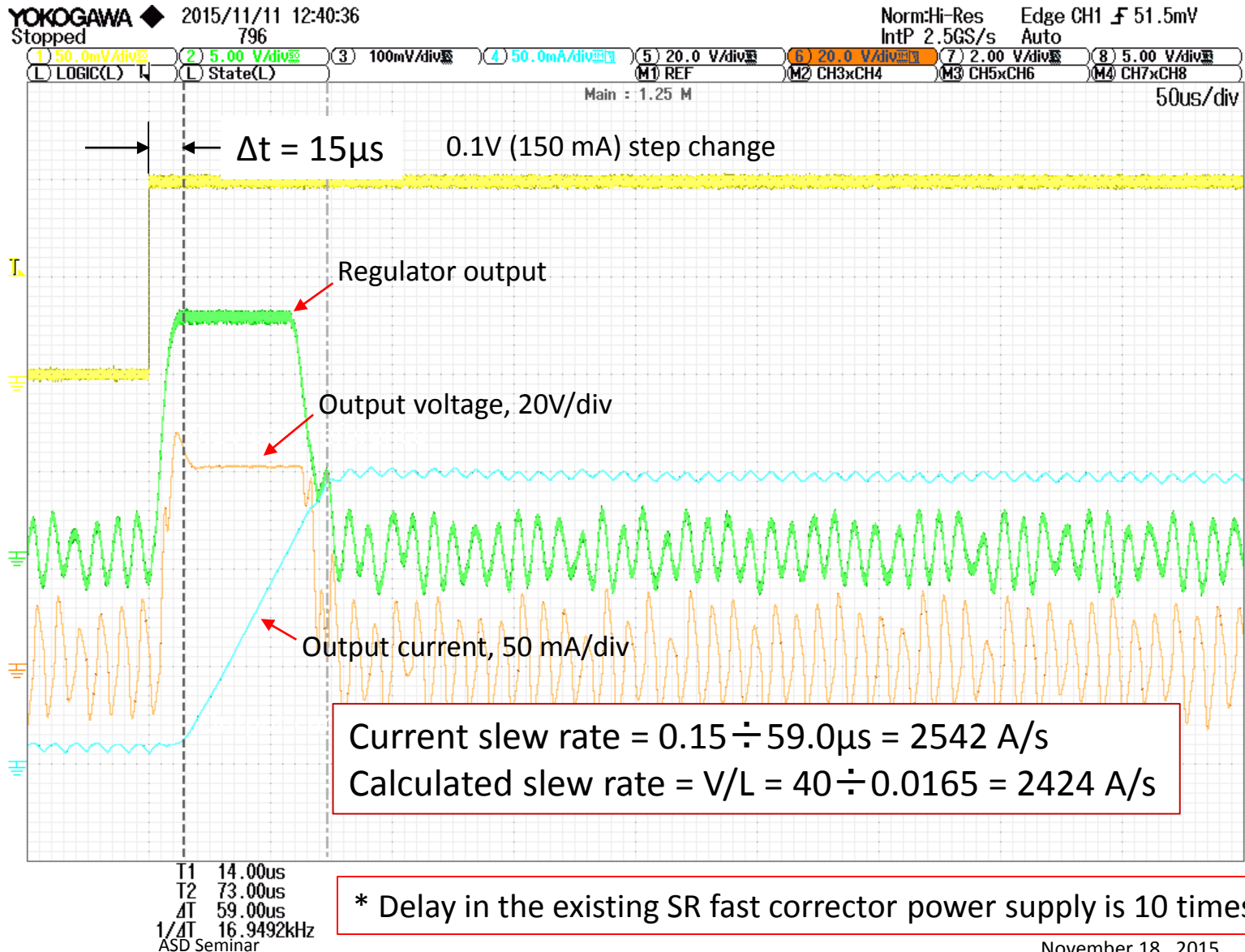

November 18, 2015

150 mA (1%) Peak-peak Reference at 1 kHz

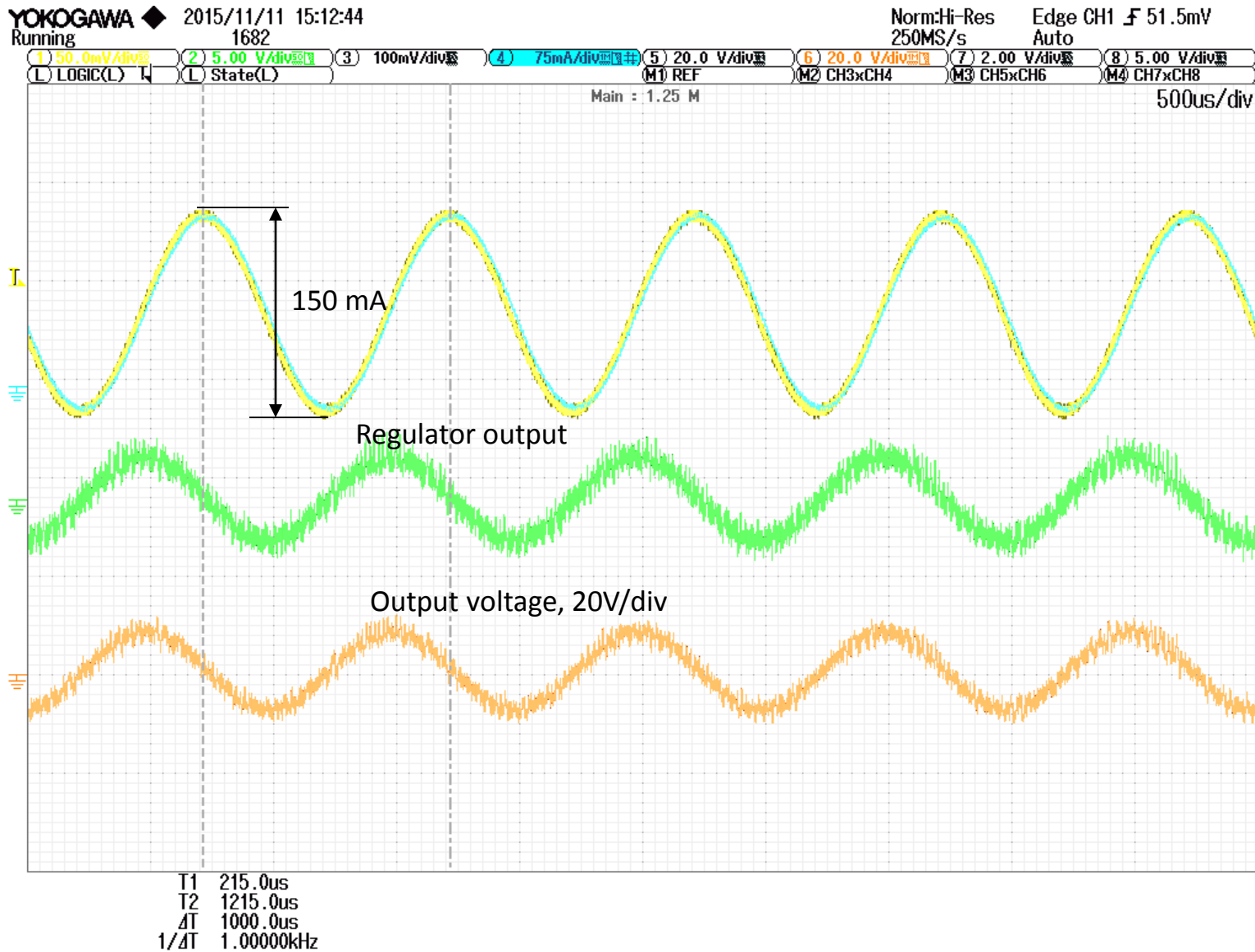

150 mA (1%) Peak-peak Reference at 5 kHz


YOKOGAWA 2015/11/11 15:30:16
Stopped 1783

Norm:Hi-Res Edge CH1 F 51.5mV
IntP 1.25GS/s Auto

1) 50.0mV/div (2) 5.00 V/div (3) 100mV/div (4) 75mA/div (5) 20.0 V/div (6) 20.0 V/div (7) 2.00 V/div (8) 5.00 V/div
L) LOGIC(L) L) State(L) M1) REF M2) CH3xCH4 M3) CH5xCH6 M4) CH7xCH8

Iain : 1.25 M

100us/div

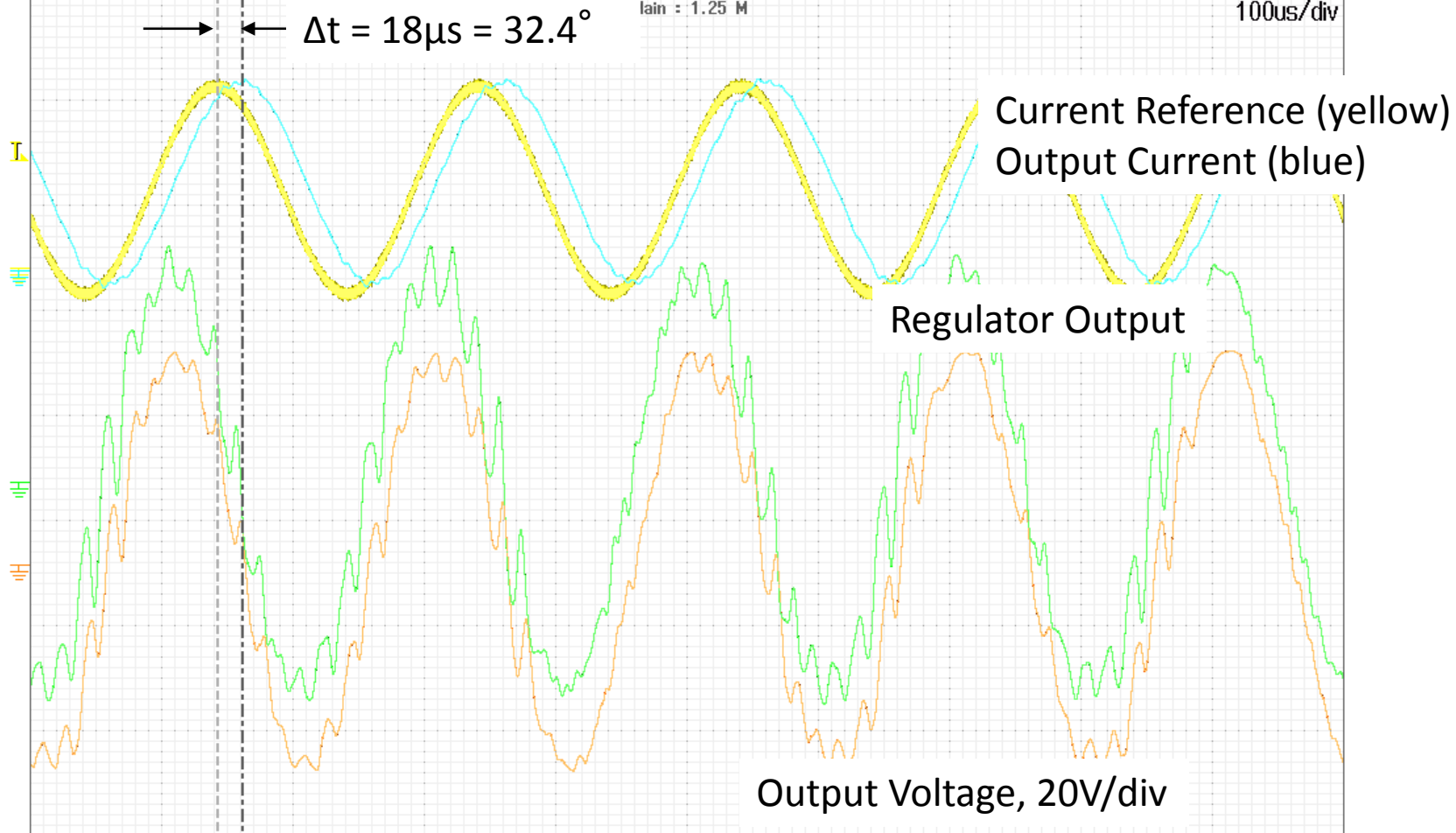


T1 43.0us
T2 61.0us
 ΔT 18.0us
1/ ΔT 55.5556kHz

150 mA (1%) Peak-peak Reference at 10 kHz

YOKOGAWA 2015/11/11 15:37:13
Stopped 1592

Norm:Hi-Res Edge CH1 \neq 51.5mV
IntP 2.5GS/s Auto

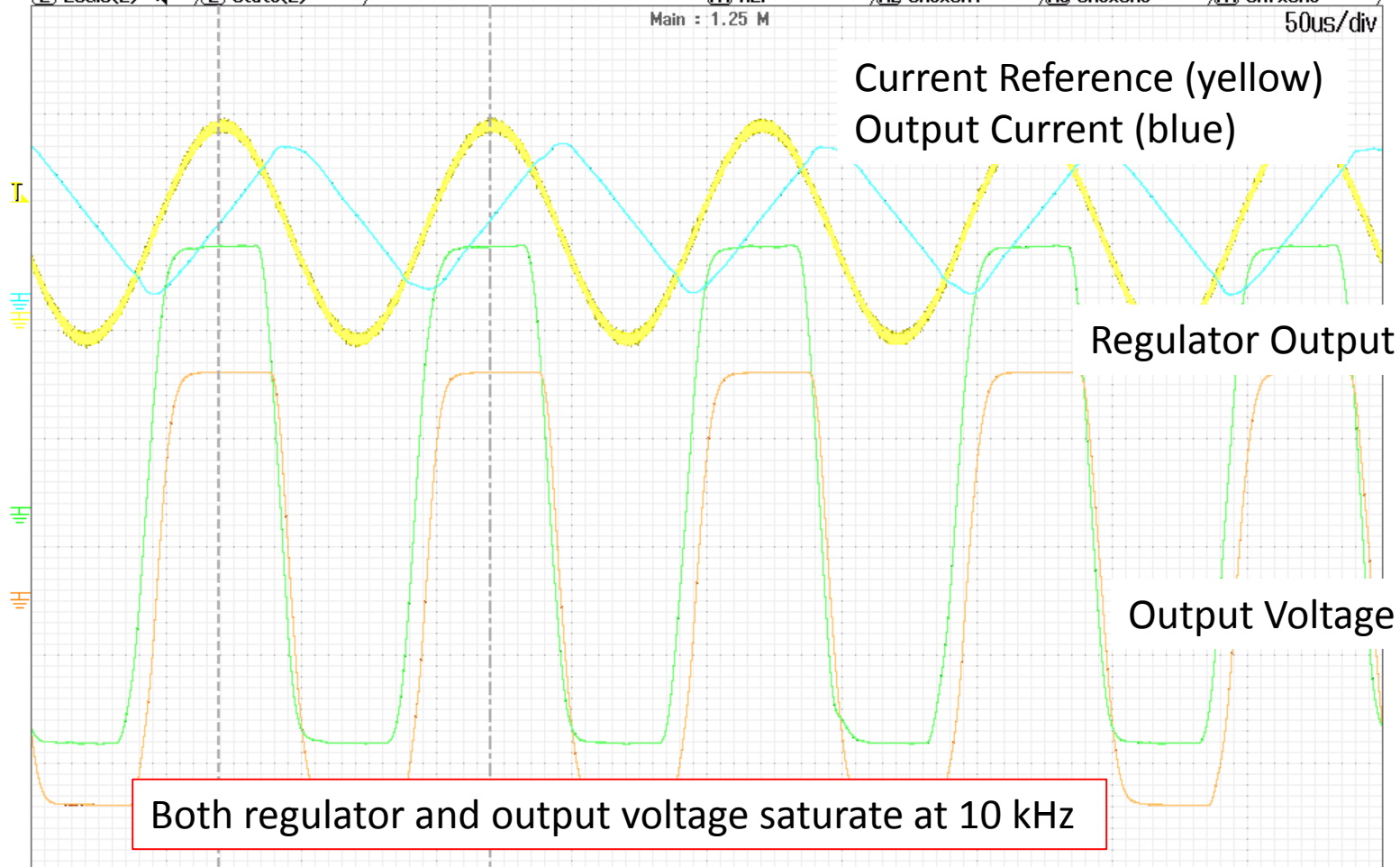
1 50.0mV/div 2 5.00 V/div 3 100mV/div 4 75mA/div 5 20.0 V/div 6 20.0 V/div 7 2.00 V/div 8 5.00 V/div
1 LOGIC(L) 2 State(L) (M1) REF (M2) CH3xCH4 (M3) CH5xCH6 (M4) CH7xCH8




T1 19.50us
T2 119.50us
 Δ T 100.00us
1/ Δ T 10.0000kHz
ASD Seminar

November 18, 2015

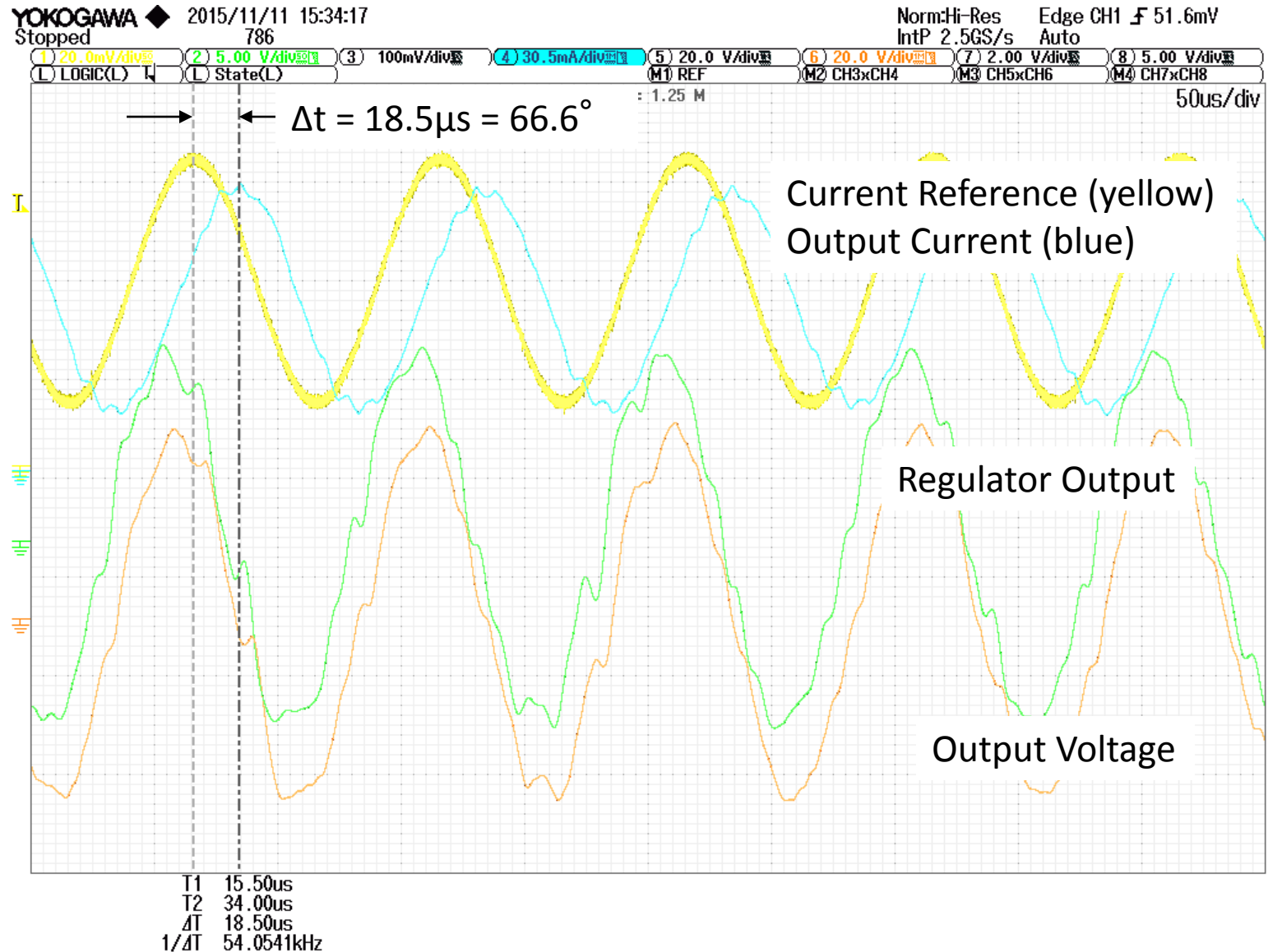75 mA (0.5%) Peak-peak Reference at 10 kHz



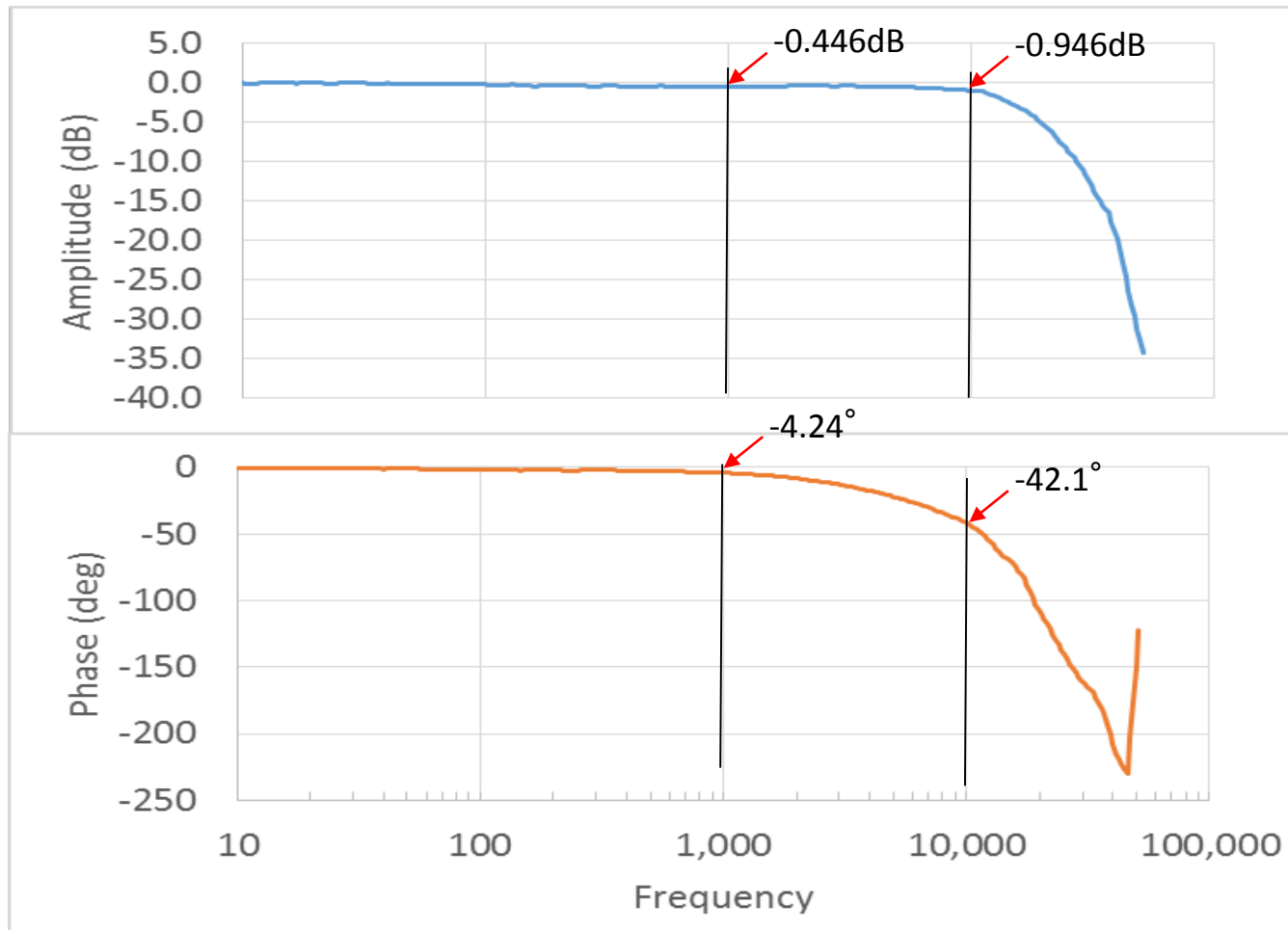Frequency Response (24.8981 mVpk, zero offset drive)



Test equipment: Dynamic signal analyzer HP35670A
24.8981 mVpk = 37.35 mApk, $\sim 1 \mu\text{rad}$ bend

Summary

- A prototype MOSFET-based fast bipolar power supply is developed
- Achieved 10 kHz bandwidth for a 0.5% small signal
- Prototype is under redesign to
 - Reduce switching noise in the circuit
 - Clean up the mistakes
- Retune control loop parameters for real magnet, which is a laminated magnet and may have a very different characteristic at high frequency



Questions?